
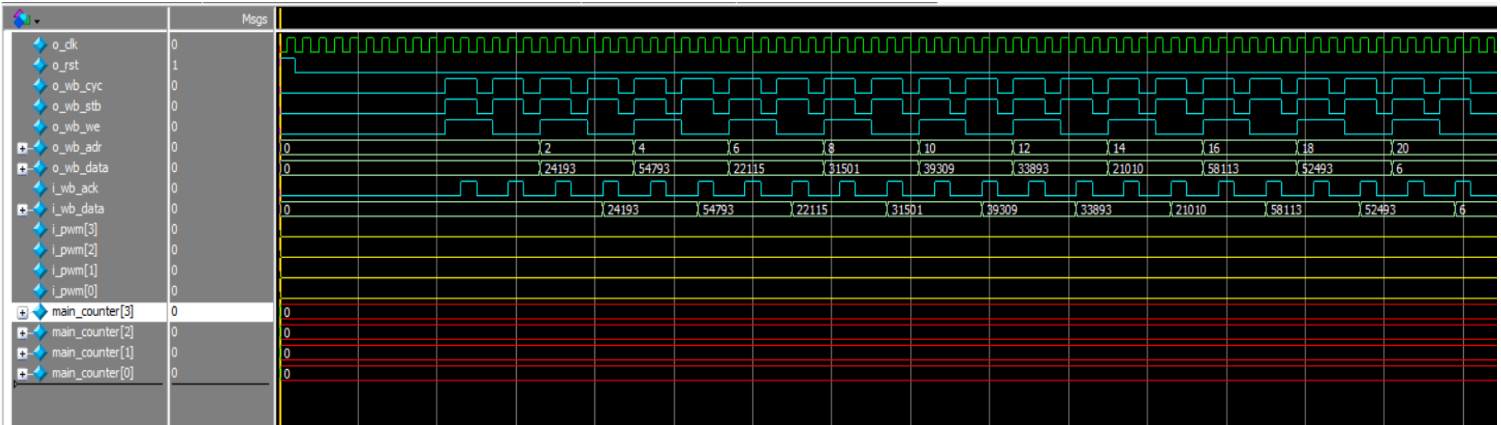


Simulation Results


Wishbone read/write operations:

 

PWM output for DC=50%:




PWM output for DC=25%:

 

Timer Mode interrupt generation and clearing:


One shot:
 
```
? INTERRUPT GENERATED! Period: 187
? INTERRUPT CLEARED! Period: 187
```




Continuous:
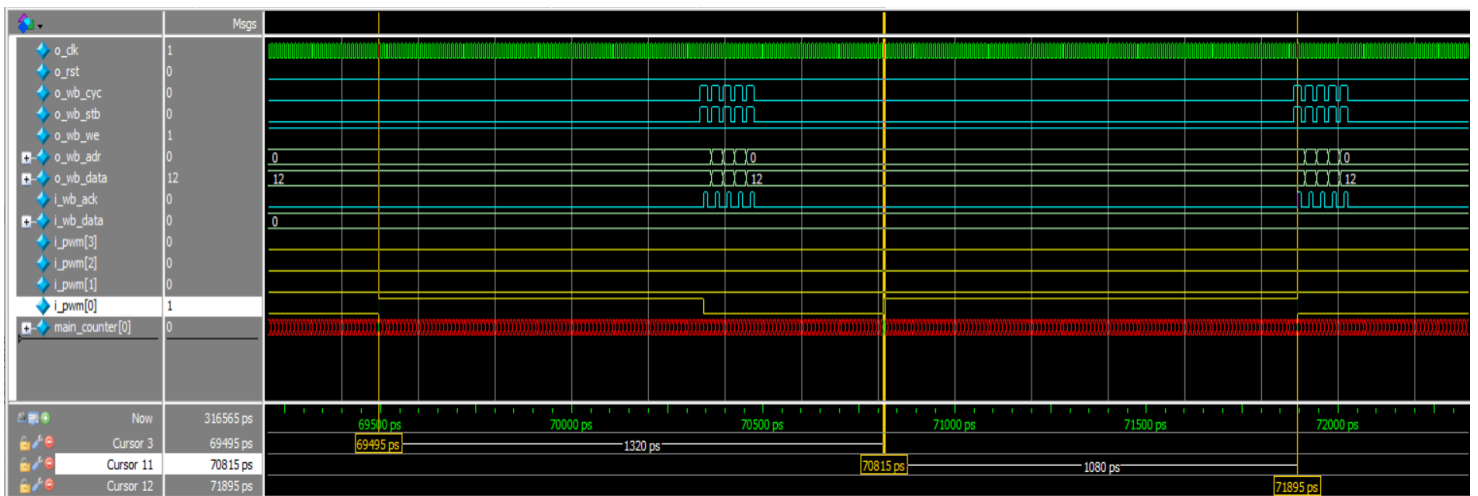
```
? INTERRUPT GENERATED! Period: 131
? INTERRUPT CLEARED! Period: 131
```




Down Clocking with Divisor=2:

 Testing Down Clocking
Testing Down Clocking with Divisor = 2 , timer mode
? INTERRUPT GENERATED! Period: 20 , divisor: 2



Down Clocking with Divisor=10:

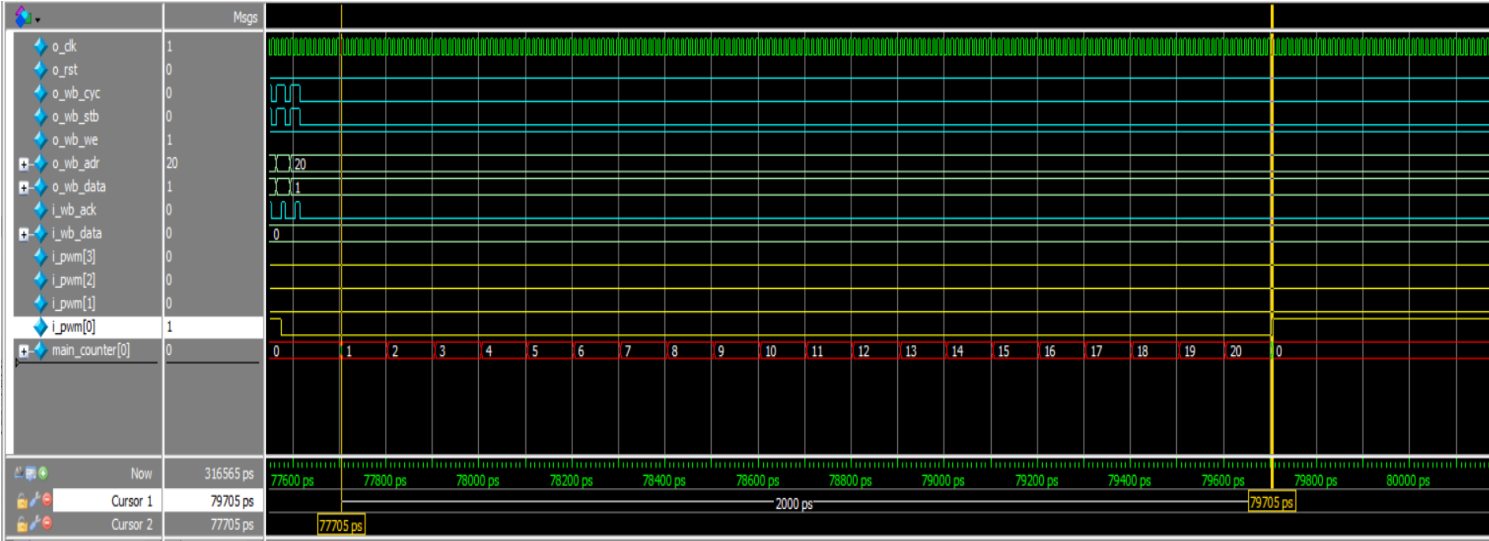
Testing Down Clocking with Divisor = 10 , timer mode
? INTERRUPT GENERATED! Period: 20 , divisor: 10



Additional Features :


DC > Period:

 Testing Edge Cases
Sub-test: Duty Cycle > Period
Expected: PWM should be always HIGH



invalid Divisor:

 Sub-test: Divisor = 0
Expected: Should work as Divisor = 1



Multi-Channel PWM:

- $i_pw[0]$ & $i_pw[1]$ has the same period = 200 but different duty cycle $DC[0]=100$ & $DC[1]=50$, as shown by purple cursor.
- $i_pw[2]$ has period = 100 & $DC[2]=25$, $i_pw[3]$ has period = 50 & $DC[3]=20$.

